

CHAPTER 4

Basic Circuit Concepts

36

- 4-1 Four measurable circuit quantities
- 4-2 Voltage
- 4-3 Current
- 4-4 Resistance
- 4-5 Watts
- 4-6 A simple electric circuit
- 4-7 Open circuits and closed circuits
- 4-8 The schematic diagram
- 4-9 Basic circuit notation
- 4-10 The short circuit
- 4-11 Electrical safety
- 4-12 *National Electrical Code*[®]

CHAPTER 5

Scientific Notation and Metric Prefixes

50

- 5-1 Rationale for studying this unit
- 5-2 Powers of 10
- 5-3 Scientific notation
- 5-4 Significant digits
- 5-5 Rounding off to three significant digits
- 5-6 Metric prefixes
- 5-7 Multiplication and division with powers of 10

CHAPTER 6

Electrical Quantity Measurement

64

- 6-1 Types of meters
- 6-2 Ammeter and voltmeter scale interpretation
- 6-3 Ohmmeter scale interpretation
- 6-4 Electrical meter connection

CHAPTER 7

Resistance

81

- 7-1 Conductance vs. resistance
- 7-2 Resistivity of materials
- 7-3 Length of a conductor
- 7-4 Cross-sectional area (CSA) of a conductor in circular mils
- 7-5 Effect of temperature on resistance
- 7-6 The American Wire Gauge (AWG)
- 7-7 Stranded wire and cable
- 7-8 Resistors
- 7-9 Fixed resistors
- 7-10 Color code
- 7-11 Power ratings

- 7-12 Variable resistors
- 7-13 Schematic symbols

CHAPTER 8

Ohm's Law

111

- 8-1 Voltage, current, and resistance
- 8-2 Ohm's law with metric prefixes

CHAPTER 9

Electrical Power and Energy

116

- 9-1 Energy
- 9-2 Units of energy
- 9-3 Power
- 9-4 Energy and cost calculations
- 9-5 Efficiency of energy conversion
- 9-6 A practical application—resistance heating

CHAPTER 10

Series Circuits

134

- 10-1 Characteristics of series circuits
- 10-2 The voltage drop
- 10-3 Resistance and current in series circuits
- 10-4 Power consumption in series circuits
- 10-5 Calculation of series circuit quantities
- 10-6 Voltage drop on a line
- 10-7 Voltage at an open element
- 10-8 Series circuits as voltage dividers
- 10-9 The general voltage divider formula
- 10-10 Polarity considerations
- 10-11 Ground as a reference point
- 10-12 Voltage sources in series

CHAPTER 11

Parallel Circuits

162

- 11-1 The nature of parallel circuits
- 11-2 Five methods of computation
 - (1) Use of Ohm's law for computing R_T
 - (2) Use of the reciprocal equation
 - (3) A practical method
 - (4) The product over the sum formula
 - (5) A special condition: all equal resistors
- 11-3 Power dissipation in parallel circuits
- 11-4 Voltage sources in parallel
- 11-5 A practical application—kitchen range heating element
- 11-6 Current dividers

CHAPTER 12

Series-Parallel Circuits and Loaded Voltage Dividers

183

- 12-1 Simplifying series-parallel circuits
- 12-2 Kirchhoff's voltage law
- 12-3 Kirchhoff's current law
- 12-4 Loaded voltage dividers

CHAPTER 13

Conduction in Liquids and Gases

206

- 13-1 The ionization process
- 13-2 Useful chemical compounds
- 13-3 Electroplating and electrolysis
- 13-4 Gases as insulators
- 13-5 Gaseous conduction by ionization
- 13-6 Conduction and ions in nature
- 13-7 Conduction in a vacuum

CHAPTER 14

Batteries

222

- 14-1 Chemical energy: a source of emf
- 14-2 Anodes and cathodes
- 14-3 Primary cells
- 14-4 Fuel cells
- 14-5 Secondary cells
- 14-6 Maintenance-free batteries
- 14-7 Miscellaneous aspects of batteries

CHAPTER 15

Magnetism and Electromagnetism

249

- 15-1 Electricity and magnetism
- 15-2 Simple magnets
- 15-3 The magnetic field
- 15-4 Ferromagnetic materials and the magnetizing process
- 15-5 Magnetic materials and the atomic theory
- 15-6 Permanent magnets
- 15-7 Electromagnetism of a straight wire
- 15-8 Electromagnetism of a coil
- 15-9 The magnetic core in the coil
- 15-10 Magnetic quantities

CHAPTER 16

Applications of Electromagnetism

270

- 16-1 Solenoids for lateral motion
- 16-2 The electromagnetic relay
- 16-3 Magnetic vibrators and bell
- 16-4 Electromagnetism for rotational motion
- 16-5 Other applications of the motor effect
- 16-6 Electromagnetism at work

CHAPTER 17

Electrical Measuring Instruments

282

(Another Application of Electromagnetism)

- 17-1 d'Arsonval meters
- 17-2 DC ammeters
- 17-3 Multirange ammeters
- 17-4 Voltmeters
- 17-5 Ohmmeters
- 17-6 Megohmmeters
- 17-7 Wattmeters
- 17-8 Bridge circuits
- 17-9 Clamp-on meters
- 17-10 Digital multimeters

CHAPTER 18

Electromagnetic Induction

309

- 18-1 Moving coils–stationary fields
- 18-2 Moving fields–stationary coils
- 18-3 Fleming's left-hand rule for generators
- 18-4 Lenz's law
- 18-5 Induction in rotating machines

CHAPTER 19

DC Generators

322

- 19-1 Principles of DC generators
- 19-2 Armature design
- 19-3 Generator field structures
- 19-4 Armature reaction
- 19-5 Buildup of self-excited fields
- 19-6 Three types of self-excited generators
(series, shunt, and compound)

- 19-7 Separately excited generators
- 19-8 Generator calculations
- 19-9 Power losses
- 19-10 Generator data and ratings
- 19-11 Magnetohydrodynamic (MHD) generation

CHAPTER 20

Mechanical Motion from Electrical Energy

358

- 20-1 Basic motor action
- 20-2 Torque and rotary motion
- 20-3 The need for commutation
- 20-4 The need for added armature coils
- 20-5 From torque to horsepower

CHAPTER 21

DC Motors

372

- 21-1 DC machines—motor or generator?
- 21-2 The counter-emf in a motor
- 21-3 Armature windings
- 21-4 Field distortion and the need for interpoles
- 21-5 The shunt motor
- 21-6 The series motor
- 21-7 The compound motor
- 21-8 Speed control of DC motors
- 21-9 Reversal of rotation
- 21-10 Power losses
- 21-11 Permanent-magnet motors

CHAPTER 22

Starters and Speed Controllers

404

- 22-1 Trends in motor control
- 22-2 The need for reduced-voltage starting
- 22-3 Manual starters
- 22-4 Manual speed controllers
- 22-5 Starters for series motors
- 22-6 Drum controllers
- 22-7 Magnetic controllers
- 22-8 The counter-electromotive force motor controller
- 22-9 The voltage drop acceleration controller (lockout acceleration)
- 22-10 Definite time controller
- 22-11 Electronic controllers

CHAPTER 23		
Solid-State Control of DC Motors		439
23-1	The shunt field power supply	
23-2	Armature control	
23-3	Current limit	
23-4	Speed control	
CHAPTER 24		
Solving DC Networks		448
24-1	The loop current method	
24-2	The superposition theorem	
24-3	Thevenin's theorem	
24-4	Norton's theorem	
APPENDIX		471
GLOSSARY		491
SELECTED ANSWERS TO ODD-NUMBERED PROBLEMS		499
INDEX		507